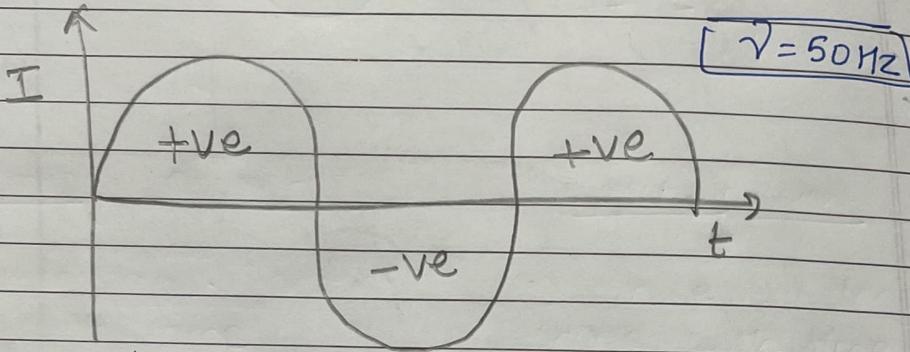




ALTERNATING CURRENT (AC)

Alternating current

A current whose magnitude changes with time and direction reversed periodically is called alternating current.



Frequency of A.C. in India is 50 Hz.

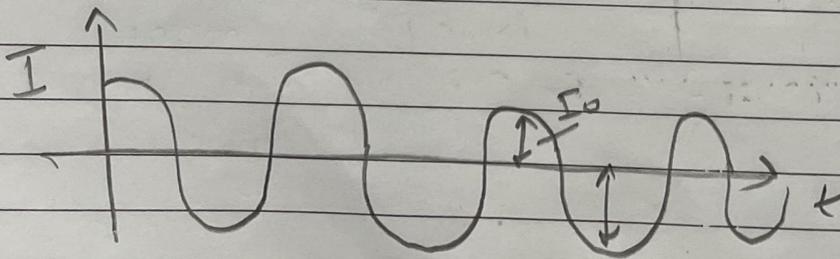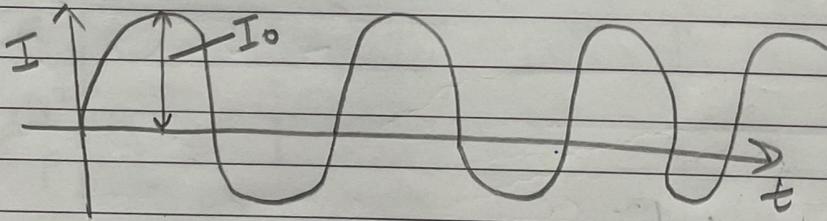

Sinusoidal graphs

Expression

$$\omega = \frac{2\pi}{T}$$

(sec)

freq.
 $\omega =$

Expression of A.C.:

$$I = I_0 \sin \omega t$$

OR

$$I = I_0 \cos \omega t$$

↓ peak value [max. amplitude]

$\omega \rightarrow$ omega

↳ angular frequency

$$[\text{SI unit} \rightarrow \frac{\text{rad}}{\text{s}}]$$

$$\boxed{\omega = \frac{2\pi}{T}}$$

rpm \rightarrow rev. per min


$$1 \text{ rpm} = \frac{2\pi \text{ rev/sec}}{60}$$

(sec) $T \rightarrow$ Time period

↳ Time taken to complete one full oscillation


freq. (ν) \rightarrow SI unit = Hz

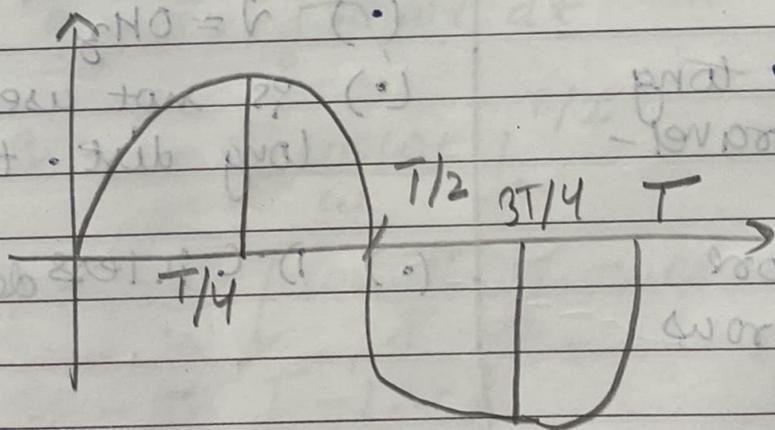↳ $\nu = \frac{1}{T}$ [Reciprocal of time period]



The graph for alternating current is symmetrical all over.

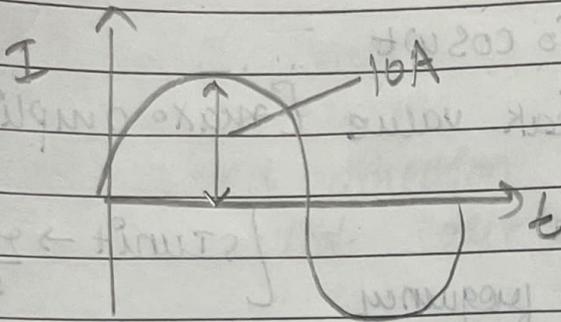Q1. In what time current will reach to 10A, when $\nu = 50 \text{ Hz}$.




$$= \frac{1}{4} \times \frac{1}{\nu}$$

$$t = \frac{1}{240} \text{ sec}$$

Alternating current


- (•) whose mag. changes with time

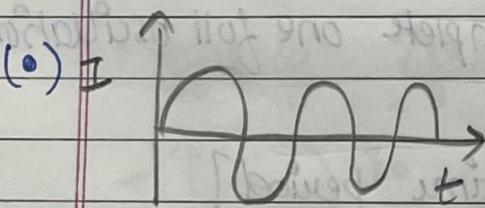

- (•) $\nu = 50 \text{ Hz}$
- (•) is used for long distance transportation
- (•) A.C. is more dangerous


Direct current

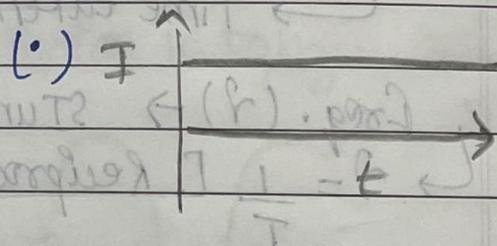- (•) whose mag. doesn't change with time



- (•) $\nu = 0 \text{ Hz}$
- (•) is not used for long dist. transportation
- (•) D.C. is less dangerous

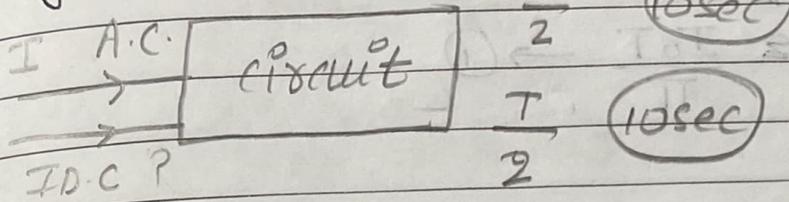(I) Average / Mean value of A.C. $T = 20 \text{ sec}$



It is that value of steady current which when pass through a circuit for half time period of A.C. produces same charge as produced by A.C. in the same circuit for the same time

for A.C.

$$I = \frac{dq}{dt}$$

$$dq = I dt$$

$$dq = I_0 \sin \omega t dt$$

$$q = \int I_0 \sin \omega t dt$$

$$q = I_0 \int_0^{T/2} \sin \omega t dt$$

$$q = -\frac{I_0 \cos \omega t}{\omega} \Big|_0^{T/2}$$

$$q = -\frac{I_0}{\omega} \left[\cos \frac{2\pi}{\pi} \frac{T}{2} - \cos 0 \right]$$

$$q = -\frac{I_0}{\omega} [-1 - 1]$$

$$q = \frac{2I_0}{\omega}$$

$$q = \frac{2 I_0 T}{\sqrt{\pi}}$$

$$q = \frac{2 I_0 T}{\pi} \rightarrow \textcircled{1}$$

For steady current (D.C.)

$$q = I t$$

$$I \rightarrow I_{av} \quad t \rightarrow T/2$$

$$q = I_{av} \times \frac{T}{2} \rightarrow \textcircled{2}$$

Comparing $\textcircled{1}$ and $\textcircled{2}$

$$\frac{I_{av} T}{2} = \frac{I_0 T}{\pi}$$

$$I_{av} = \frac{2}{\pi} I_0$$

$$I_{av} = 0.636 I_0$$

Voltage
average

$$V_{av} = \frac{2}{\pi} V_0$$


$$V_{av} = 0.636 V_0$$

Root mean

IA
→

I.D.C. = ?

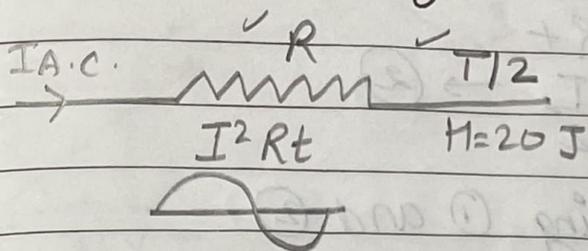Root mean square (rms) / virtual / effective value of A.C.



$I_{D.C.} = ?$ It is that value of steady current which when passed through a resistance produces same amt^o of heat as produced by A.C. in the same resistance for the same time.

$$H = I^2 R t$$

for A.C.

$$I = I_0 \sin \omega t = \sqrt{v}$$

$$dH = I_0^2 \sin^2 \omega t R dt$$

$$H = \int_0^{T/2} I_0^2 R \sin^2 \omega t dt$$

$$H = I_0^2 R \int_0^{T/2} \sin^2 \omega t dt$$

$$H = I_0^2 R \int_0^{T/2} \left(\frac{1 - \cos 2\omega t}{2} \right) dt$$

$$H = \frac{I_0^2 R}{2} \left[t - \frac{\sin 2\omega t}{2\omega} \right]_0^{T/2}$$

$$H = \frac{I_0^2 R}{2} \left[\left(\frac{T}{2} - 0 \right) - \frac{1}{2\omega} \left[\sin 2 \frac{2\pi}{T} \frac{T}{2} - \sin 0 \right] \right]$$

$$H = \frac{I_0^2 R T}{4} \rightarrow \textcircled{1}$$

For steady current

$$H = I^2 R t$$

$$H = \frac{I^2 R t}{2} \rightarrow (2)$$

Comparing (1) and (2)

$$\frac{I_0^2 R t}{4} = \frac{I^2 R t}{2}$$

$$I^2 = \frac{I_0^2}{2}$$


$$I = \frac{I_0}{\sqrt{2}} = 0.707 I_0$$

$$V = \frac{V_0}{\sqrt{2}}$$

$$V = 0.707 V_0$$


(1)

Phasor Diagrams (♥)

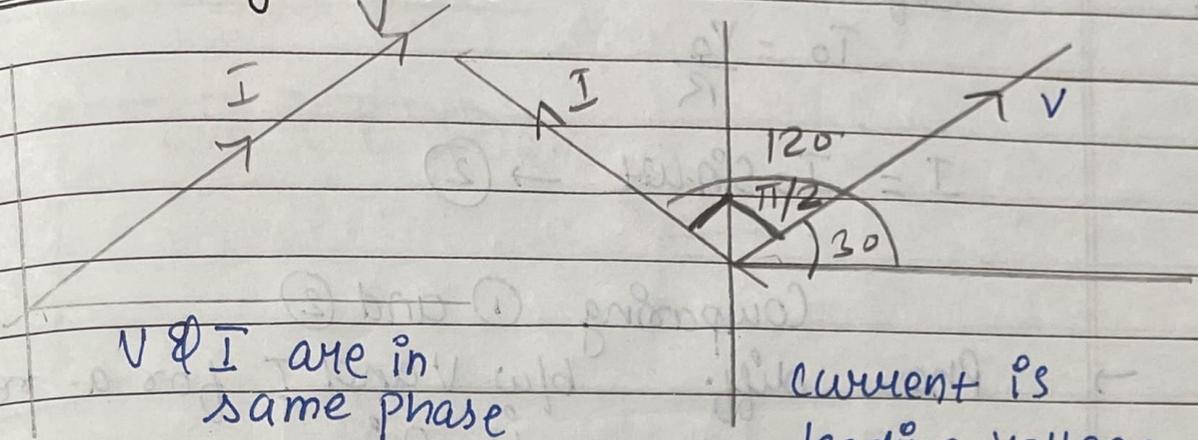


V & I are in same phase

current is leading voltage by $\pi/2$

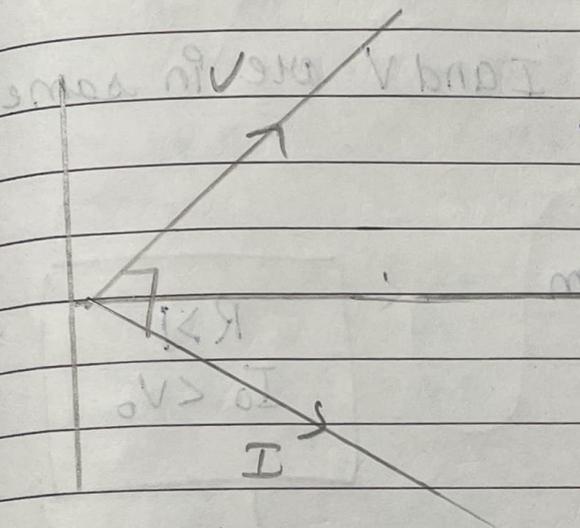

Voltage is leading current by $\pi/2$

(1) A.C. through resistance

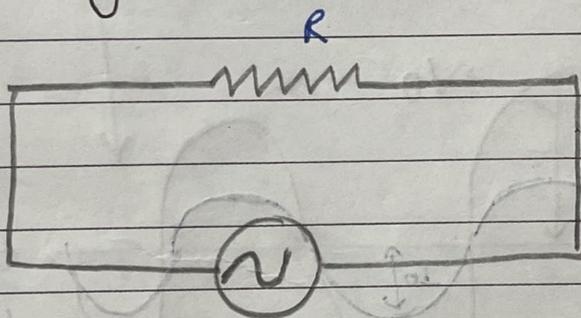

DC Battery
|||

(~) AC source

$$V = V_0 \sin \omega t$$

Given

$$V = V_0 \sin \omega t \quad \text{--- (1)}$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{V_0 \sin \omega t}{R}$$

I_f

$$I_0 = \frac{V_0}{R}$$


$$I = I_0 \sin \omega t \rightarrow (2)$$

Comparing ① and ②

→ Phase diff. b/w V and I for a resistance is 0°


→ For a resistance I and V are in same phase

Phasor diagram

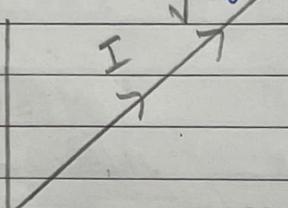

$$R > 1$$


$$I_0 < V_0$$

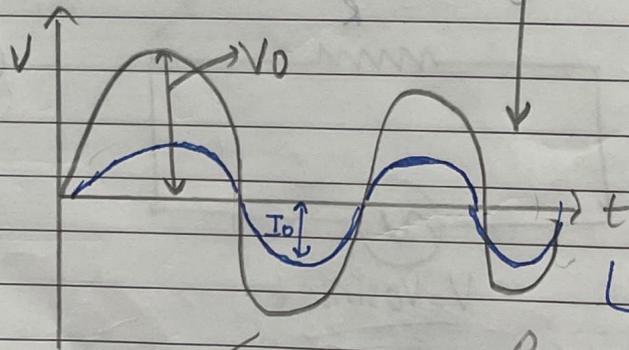

$I_0 < V_0$

$R > 1$
 $V = I R$
 $V = I$

(2) A.C. through

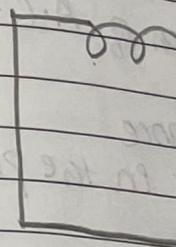

Given

$V = E$

$V =$

$V = L \frac{dI}{dt}$

$I =$

$I =$

$I =$

$I =$


$I =$

wh

wh

A.C. through inductor

(2)

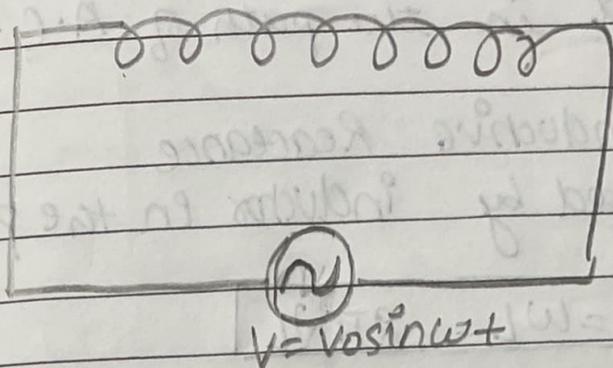

Given

$$V = V_0 \sin \omega t$$

$$V = E = - \left| \frac{d\Phi}{dt} \right| \quad (V \& \Phi \text{ both included})$$

$$V = L \frac{dI}{dt}$$

$$\frac{V dt}{L} = dI$$

$$dI = \frac{V_0 \sin \omega t}{L} dt$$

$$I = \int \frac{V_0}{L} \sin \omega t dt$$

$$I = \frac{V_0}{L} \int \sin \omega t dt$$

$$I = \frac{V_0}{L} \left(\frac{-\cos \omega t}{\omega} \right)$$

$$I = - \left(\frac{V_0}{\omega L} \right) \cos \omega t$$

$$I = -I_0 \cos \omega t \rightarrow (2)$$

$$\text{where } I_0 = \frac{V_0}{\omega L} \rightarrow (3)$$

$$\omega L = \frac{2\pi}{T} \frac{V dt}{dI} = \frac{V_s}{S I} = \frac{\text{Volt}}{A}$$

$$\omega L = \Omega$$

$$\omega L = X_L$$

$X \rightarrow$ reactance (Ω)

Reso. offered in the path of A.C.


$X_L (\Omega) \rightarrow$ Inductive Reactance

\hookrightarrow Reso. offered by inductors in the path of A.C.

$$X_L = \omega L = 2\pi fL$$

$$X_L = \omega L$$

$$X_L = 2\pi fL$$

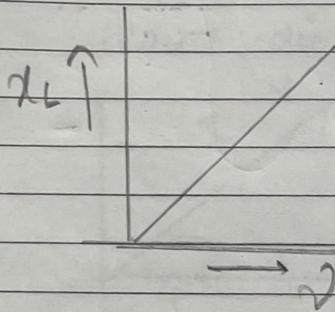




$$I_0 = \frac{V_0}{\omega L} = \frac{V_0}{X_L}$$

$$V_0 = I_0 X_L$$

$V_r = I_r X_L$ Ohm's law for inductor


$$I_r = \frac{V_r}{X_L} = \frac{V_r}{2\pi fL}$$

IV: current

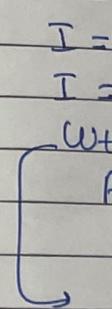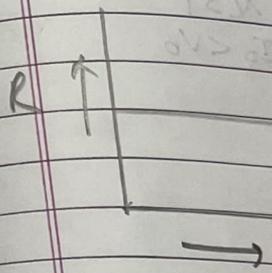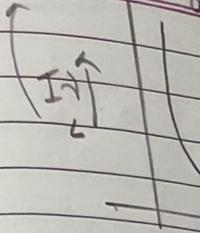

$I \propto$ current of L (inductor)


(Current of Inductor)

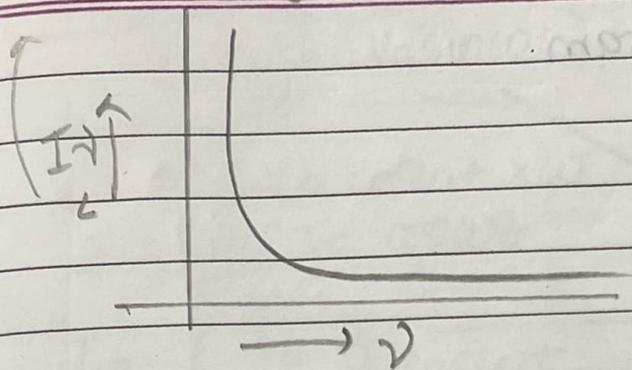

It also depends on frequency

Contrary

(Resistance is independent of frequency)

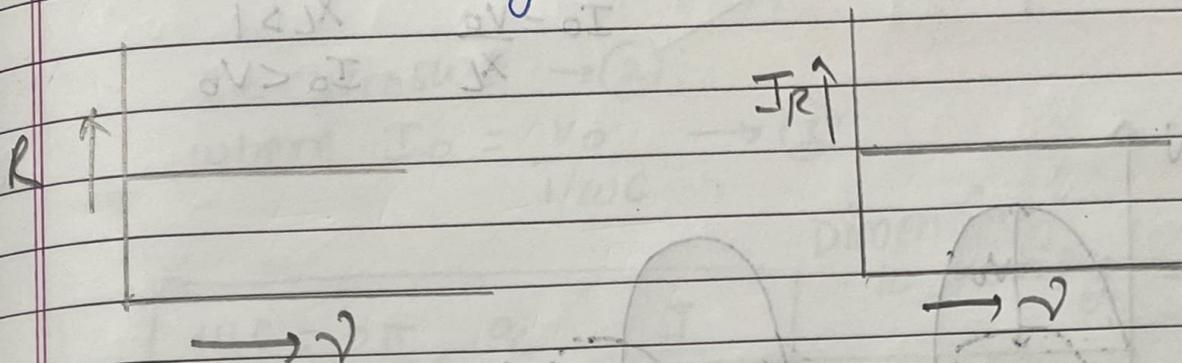

$$V = V_0 \sin(\omega t)$$

$$I = -I_0 \cos \omega t \rightarrow (4)$$

$$I = -I_0 \sin(90 - \omega t)$$

ωt is taken as a std. reference

Anything will be subtracted from (ωt)

$$I = I_0 \sin(\omega t - \frac{\pi}{2}) \rightarrow (5)$$


We know

$$V = V_0 \sin \omega t \rightarrow (6)$$

comparing (5) and (6)


- phase diff. b/w V & I is $\pi/2$
- Voltage leads current by $\pi/2$
- current lags behind voltage by $\pi/2$

Phasor Diagram

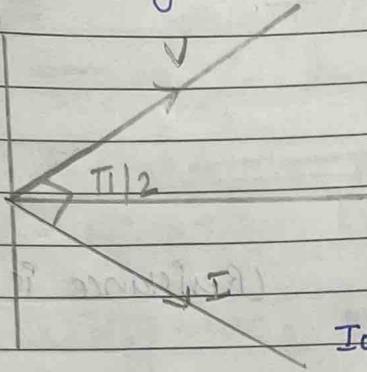


$$I_0 = \frac{V_0}{X_L} \quad X_L > 1$$

$$I_0 < V_0$$

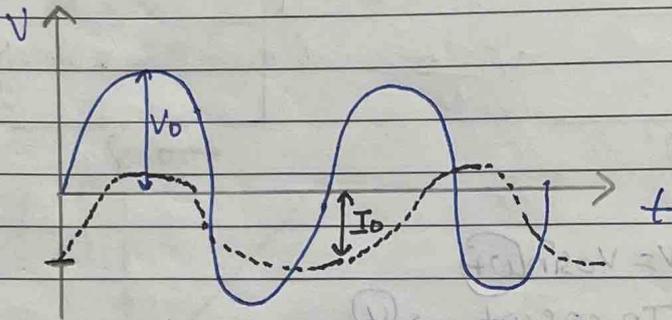

(3) A.C. through capacitor

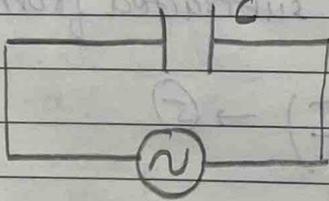

Given $V = V_0 \sin \omega t \rightarrow (1)$

using $q = CV$

Diff. w.r.t time

$$\frac{dq}{dt} = C \frac{dv}{dt}$$

$$I = C \frac{dv}{dt}$$

$$I = C \frac{d(V_0 \sin \omega t)}{dt}$$

$$I = C V_0 \cos \omega t \times \omega$$

$$I = \omega C V_0 \cos \omega t$$

$$I = \left(\frac{V_0}{\left(\frac{1}{\omega C}\right)} \right) \cos \omega t$$

$$I = I_0 \cos \omega t \rightarrow (2)$$

$$\text{where } I_0 = \frac{V_0}{1/\omega C} \rightarrow (3)$$

$$\omega C = \frac{2\pi}{T} \times \frac{q}{V} = \frac{I}{V}$$


$$\frac{1}{\omega C} = \frac{V}{I} = R (\Omega)$$

Dimension
to verify $\frac{1}{\omega C} = \Omega$

$$\frac{1}{\omega C} = X_C$$

$X_C \rightarrow$ Capacitive reactance (Ω)
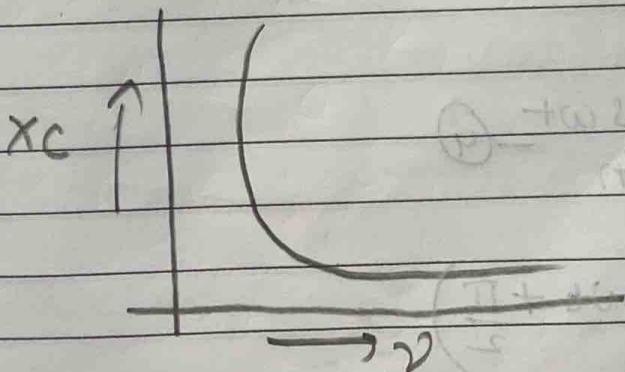
$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \nu C}$$



Using

$$I_0 = \frac{V_0}{\frac{1}{\omega C}}$$

$$I_0 = \frac{V_0}{X_C}$$

$$V_0 = I_0 X_C$$

$$V_r = I_r X_C$$


Ohm's law for a capacitor

$$I_r = \frac{V_r}{X_C}$$

$$I_r = \frac{V_r}{\frac{1}{\omega C}}$$

$$I_r = V_r \omega C$$

$$I_r \propto V_r$$

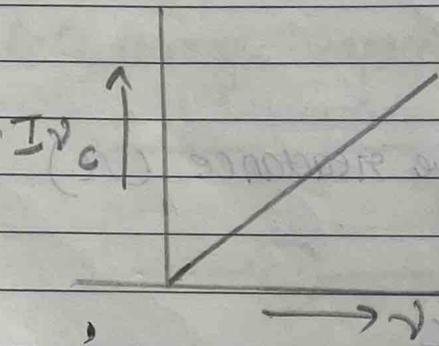eqⁿ (2)

$$I = I_0 \cos \omega t \quad (4)$$

$$V = I_0 \sin \omega t$$

$$I = I_0 \sin \left(\omega t + \frac{\pi}{2} \right)$$

using

$$v = V_0 \sin \omega t \rightarrow (5)$$

Comparing (4) and (5)


For a capacitor

Phase diff. b/w v and i is $\pi/2$


Current leads vol by $\pi/2$

voltage lags behind i by $\pi/2$

Phasor Diagram

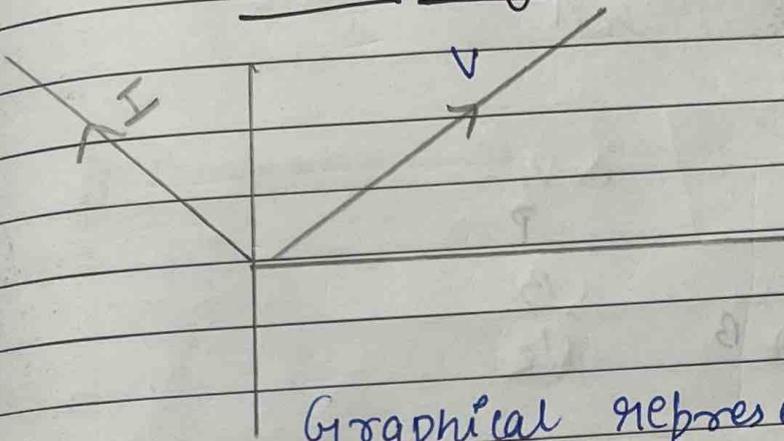

Graphical representation

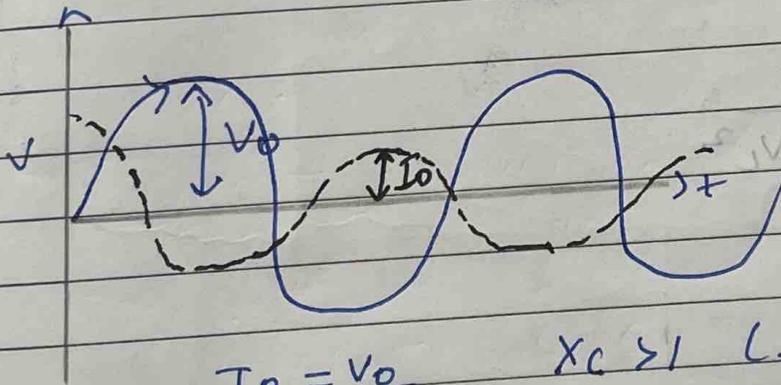


$$I_0 = \frac{V_0}{X_C}$$

$$X_C > 1 \quad (I_0 < V_0)$$


always like this

(4) A.C. through LR circuit

V → divide

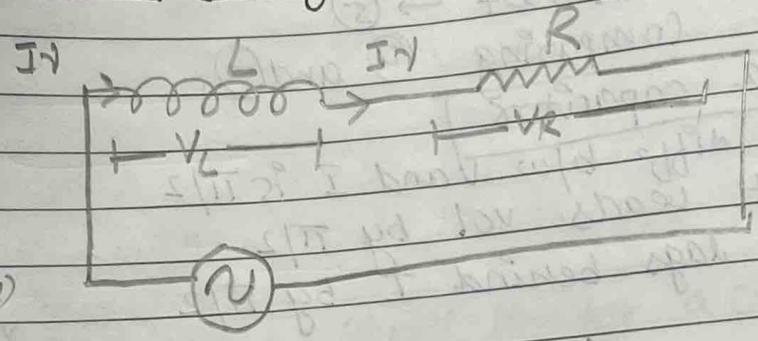

(Inductor voltage lead by 90°)

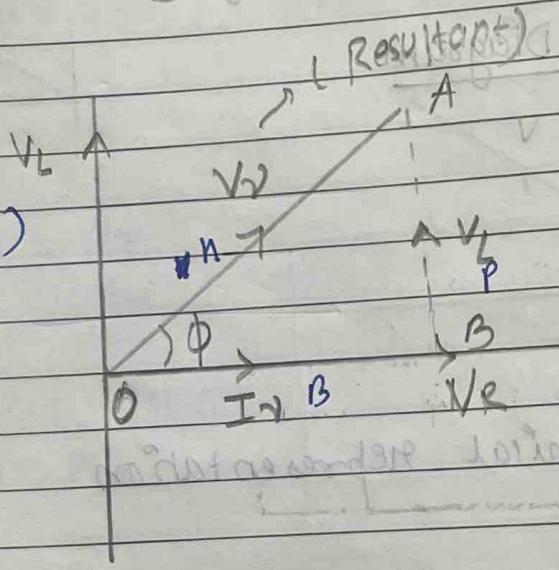

(5)

In ΔABO

$$V_v = \sqrt{V_R^2 + V_L^2}$$

$$V_R = I_v R$$

$$V_L = I_v X_L$$

$$V_v = \sqrt{(I_v R)^2 + (I_v X_L)^2}$$

$$V_v = I_v \sqrt{R^2 + X_L^2}$$

$$V_v = I_v Z$$

Z → impedance (Ω)

for LR circuit



$$Z = \sqrt{X_L^2 + R^2}$$

Resistance offered by more than one component in the path of A.C.

$$\tan \phi = \frac{V_L}{V_R} = \frac{I_0 X_L}{I_0 R}$$

$$\tan \phi = \frac{X_L}{R}$$

(5) A.C. through CR circuit

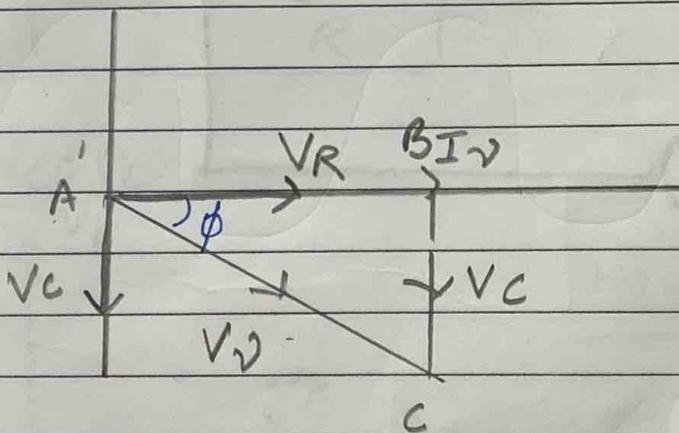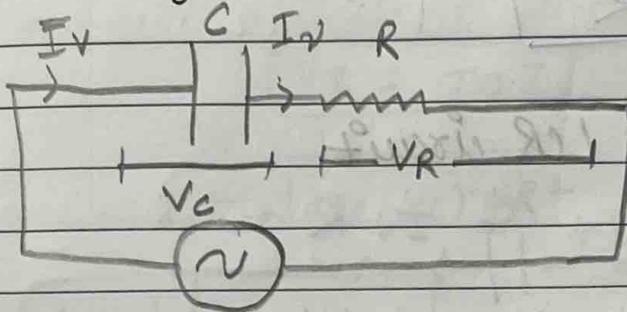

In ΔABC

$$V_v = \sqrt{V_c^2 + V_R^2}$$

$$V_R = I_v R$$

$$V_c = I_v X_c$$

$$V_V = \sqrt{(I_V R)^2 + (I_V X_C)^2}$$

$$V_V = I_V \sqrt{R^2 + X_C^2}$$

$$V_V = I_V Z$$



(2) $Z \rightarrow$ Impedence

$$Z = \sqrt{X_C^2 + R^2}$$

$$\tan \phi = \frac{V_C}{V_R} = \frac{I_V X_C}{I_V R}$$

$$\tan \phi = \frac{X_C}{R}$$

(6) A.C. through LCR circuit

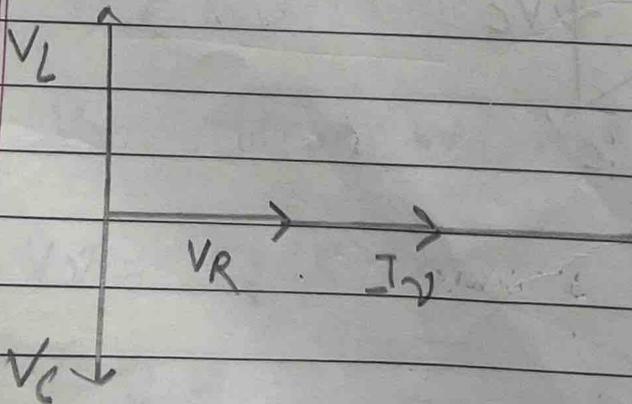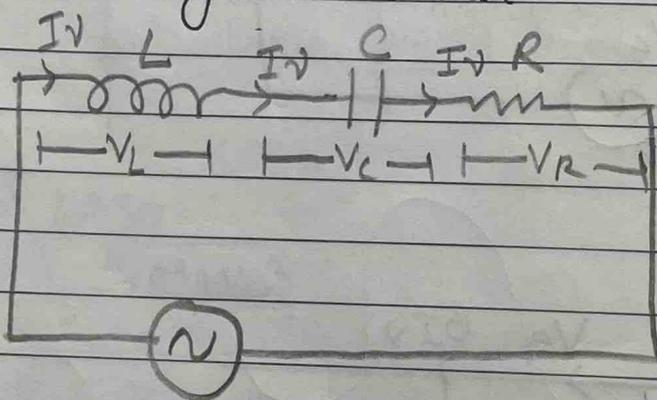


Ans
(1)

(11)

What is phase angle b/w inductive voltage and capacitive voltage in series in LCR?

π (180°)

(i) Ans

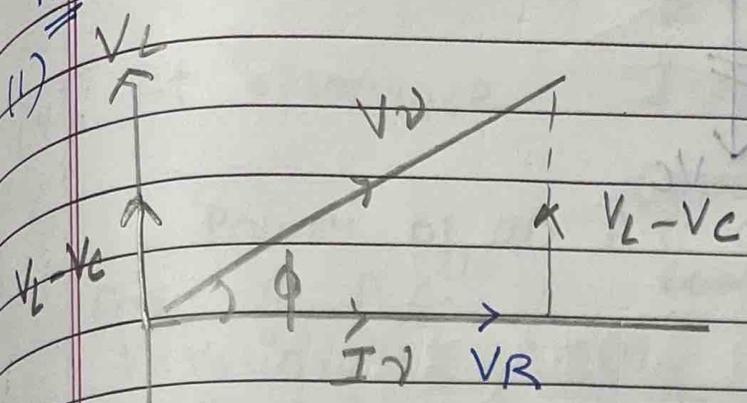

$$V = \sqrt{(V_L - V_C)^2 + V_R^2} = IZ$$


$$V = I \sqrt{(X_L - X_C)^2 + R^2}$$

$$V = IZ$$

$$Z = \sqrt{(X_L - X_C)^2 + R^2}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

(ii)

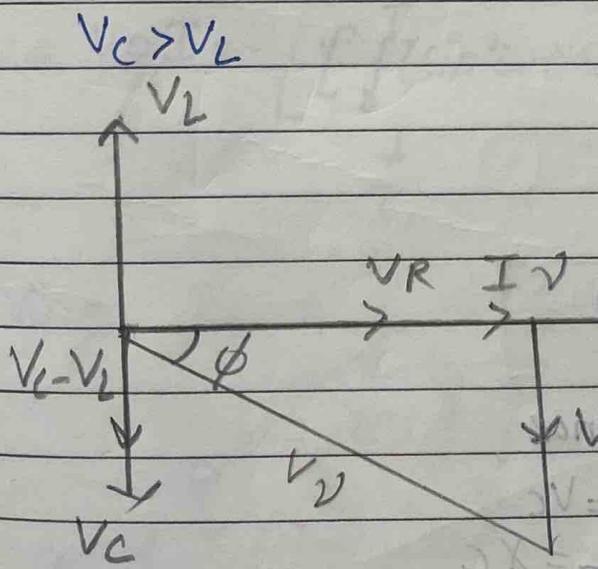

$$V = \sqrt{(V_C - V_L)^2 + V_R^2}$$


$$V = I \sqrt{(X_C - X_L)^2 + R^2}$$

Z (Impedance)

$$V = IZ$$

$$Z = \sqrt{(X_C - X_L)^2 + R^2}$$

$$\tan \phi = \frac{X_C - X_L}{R}$$

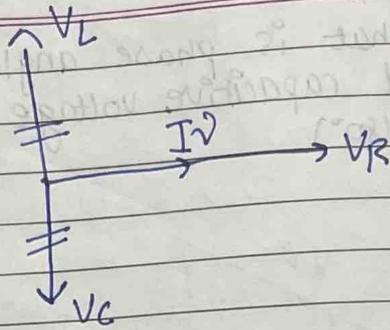(iii) case $V_L = V_C$ 

#

$$V_L = V_C$$

$$I \omega X_L = I \omega X_C$$

$$\boxed{X_L = X_C}$$

$$\boxed{\omega L = \frac{1}{\omega C}}$$

This happens at a particular frequency called resonant frequency

$$\omega = \omega_0$$

Angular resonant frequency

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\boxed{f_0 = \frac{1}{2\pi \sqrt{LC}}}$$

Resonant frequency

At resonance

(i) $V_L = V_C$

(ii) $X_L = X_C$

(iii) $Z \rightarrow$ impedance

$$Z = \sqrt{X_L^2 + X_C^2}$$

(iv)

current

(v)

At reson

Power

For an

$$V = V_0 \sin \omega t$$

$$I = I_0 \sin \omega t$$

 $\phi \rightarrow$ phase

$$dw = V di$$

$$dw = V I dt$$

$$dw = V_0 I_0 dt$$

$$dw = V_0 I_0 dt$$

$$dw = V_0 I_0 dt$$

$$\omega = V_0 I_0$$

$$\omega = V_0 I_0$$

Solving

$$= C$$

$$= C$$

$$= \frac{\cos \phi}{2} \left[\frac{T}{2\omega} \left(\frac{\sin 2\omega T}{T} - \sin 0 \right) \right]$$

$$= I_1 = \frac{\cos \phi}{2} T \rightarrow \textcircled{4}$$

Solving I_2

$$\sin \phi \int_0^T \sin \omega t \cos \omega t dt$$

• Multiply and divide by 2

$$I_2 = \sin \phi \int_0^T \frac{2 \sin \omega t \cos \omega t}{2} dt$$

$$I_2 = \sin \phi \int_0^T \frac{\sin 2\omega t}{2} dt$$

$$I_2 = \frac{\sin \phi}{2} \left[\frac{-\cos 2\omega t}{2\omega} \right]_0^T$$

$$I_2 = -\frac{\sin \phi}{4\omega} \left[\cos 2 \frac{2\pi}{T} T - \cos 0 \right]$$

$$I_2 = -\frac{\sin \phi}{4\omega} [1 - 1]$$

$$I_2 = 0$$

Put I_1 and I_2 in $\textcircled{3}$

$$W = I_0 V_0 \left[\frac{\cos \phi T}{2} + 0 \right]$$

$$W = I_0 V_0$$

$$W = V_0 I_0 \frac{\cos \phi T}{2}$$

$$\frac{W}{T} = \frac{V_0 I_0 \cos \phi}{2}$$

Inductor
Ideal

$$P = \frac{V_0 I_0 \cos \phi}{\sqrt{2} \sqrt{2}}$$

$$\boxed{P = V_r I_r \cos \phi} \quad \cos \phi \rightarrow \text{power factor (P.F.)}$$

Case I: for a resistance

$$\phi = 0^\circ$$

$$\text{P.F. } \cos \phi = \cos 0^\circ = 1$$

$$P = E_r I_r \cos \phi$$

$$\boxed{P = E_r I_r}$$

Case II: for an inductor

$$\phi = \pi/2$$

$$\text{P.F. } \cos \phi = \cos \pi/2 = 0$$

$$P = E_r I_r \cos \phi$$

$$\boxed{P = 0}$$

Ideal Inductor Pure inductive circuit consumes zero power.

Case III: For a capacitor

$$\phi = \pi/2$$

$$\text{P.F.} = \cos \phi = 0$$


$$\boxed{P = 0}$$

pure capacitor consumes zero power.

Case IV: LR

$$\tan \phi = \frac{X_L}{R}$$

Impedance triangle

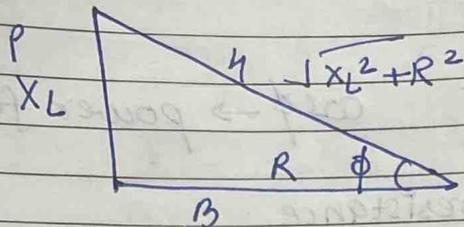

$$\cos \phi = \frac{R}{\sqrt{X_L^2 + R^2}} = \boxed{\frac{R}{Z}}$$

$$P = V_r I_r \cos \phi$$

$$P = V_r I_r \frac{R}{Z}$$

$$P = V_r \left[\frac{V_r}{Z} \right] \frac{R}{Z}$$

$$P = \frac{V_r^2 R}{Z^2}$$


$$P = \frac{V_r^2 R}{(X_L^2 + R^2)}$$

Case - V

CR Circuit

$$\tan \phi = \frac{X_C}{R}$$

Impedance Δ

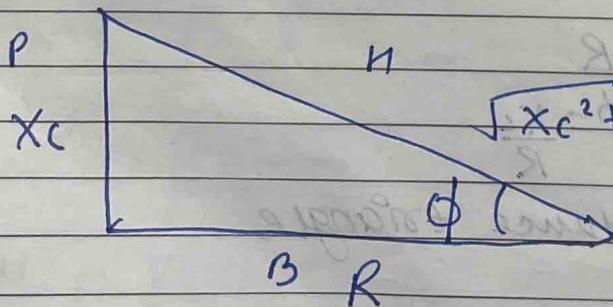

$$\cos \phi = \frac{R}{\sqrt{X_C^2 + R^2}} = \frac{R}{Z}$$

$$P = V I \cos \phi$$

$$P = V I \frac{R}{Z}$$

$$P = V \left[\frac{V}{Z} \right] \frac{R}{Z}$$

$$P = \frac{V^2 R}{Z^2}$$

$$P = \frac{V^2 R}{(X_C^2 + R^2)}$$

Case VI $L < CR$

(a) $V_L > V_C$ $\tan \phi = \frac{X_L - X_C}{R}$

$$\cos \phi = \frac{R}{\sqrt{(X_L - X_C)^2 + R^2}}$$

$$\cos \phi = \frac{R}{Z}$$

$$P = V I \cos \phi$$

$$= V I \frac{R}{Z}$$

$$= V \left[\frac{V}{Z} \right] \frac{R}{Z}$$

$$= \frac{V^2 R}{Z^2} = \frac{V^2 R}{(X_L - X_C)^2 + R^2}$$

(b)

$$V_C > V_L$$

$$\tan \phi = \frac{X_C - X_L}{R}$$

$$\cos \phi = \frac{R}{\sqrt{(X_C - X_L)^2 + R^2}}$$

$$\cos \phi = \frac{R}{Z}$$

$$P = V I \cos \phi$$

$$= V I \frac{R}{Z}$$

$$= V I \left[\frac{V}{Z} \right] \frac{R}{Z}$$

$$= \frac{V^2 R}{Z^2} = \frac{V^2 R}{(X_C - X_L)^2 + R^2}$$

(c) LCR $V_L = V_C$ $\tan \phi = 0$

$$\phi = 0^\circ \quad \boxed{\cos \phi = 1}$$

At resonance p.f. is unity

Wattless current: A current which when flows in a circuit consume zero power is called wattless current. eg. current in inductor or capacitor leads to 0 power consumption.

$$P = V I \cos \phi$$

$$\phi = \pi/2 \quad \boxed{P=0}$$

Q1. Capacitor blocks D.C. How?

$$X_C = \frac{1}{\omega C}$$

$$X_C = \frac{1}{2\pi f C}$$

$$\text{D.C. } \boxed{f=0} \Rightarrow X_C = \frac{1}{0}$$

$$X_C = \infty \quad \boxed{I=0}$$

Since it offers ∞ resistance, current becomes 0, hence we say capacitor blocks D.C.

What will


Q1.

Q2.

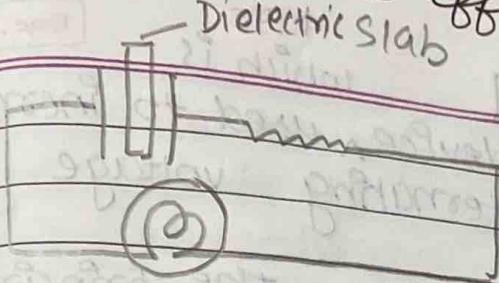Q3.


Permea

What will be the effect on brightness of bulb?



Die-slab \uparrow
 $X_c = \frac{1}{\omega C}$ $X_c = \downarrow$
 $I = \uparrow$
 Brightness \uparrow

Q2:

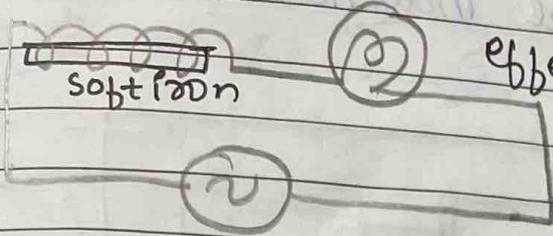



effect on brightness of bulb after inserting soft iron?

solⁿ: $\mu \uparrow$
 $L = \mu n^2 A d$

$X_L = \omega L$ $X_L \uparrow$ $I \downarrow$ Brightness \downarrow
 permeability \uparrow , mag. field lines \uparrow , $\phi_m \uparrow$, induced current \uparrow

Brightness \downarrow ← opposes the cause

Q3:

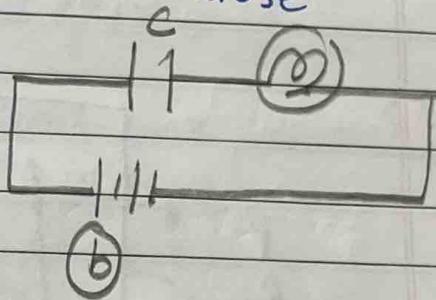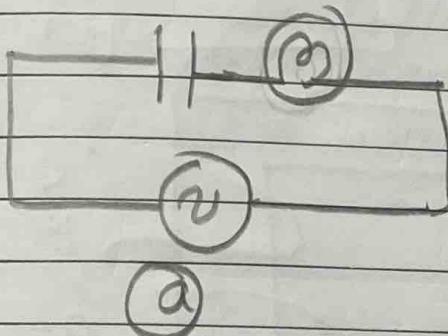

If v is red, what will effect on brightness in both cases?

solⁿ:

(b) $\rightarrow v = 0$ $C \rightarrow$ blocks DC current
 Bulb will not glow

(a) $\rightarrow v \uparrow$ $X_c = \frac{1}{\omega C} = \frac{1}{2\pi v C}$ $v \uparrow, X_c \downarrow, I \uparrow$
 Brightness \uparrow

✓ 5 markers

Page No.



Date:

TRANSFORMER which is


USE: It is a device used to increase or decrease alternating voltage

PRINCIPLE: It is based on the principle of mutual induction

CONSTRUCTION:

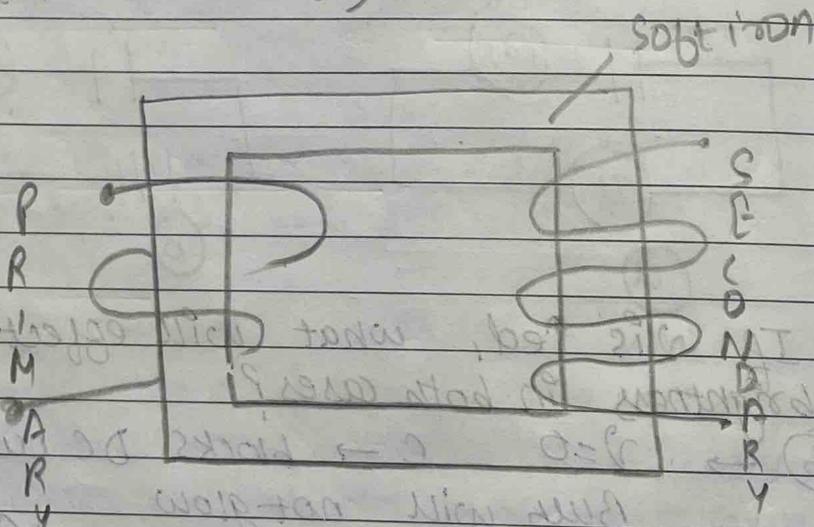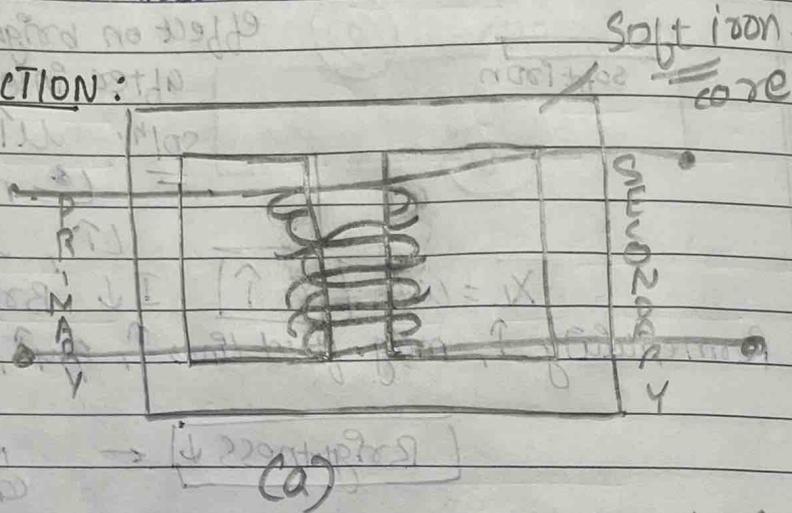

WORKING:

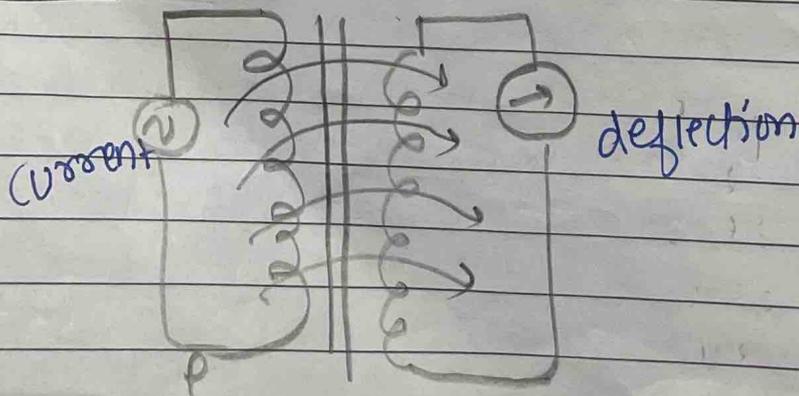

change in
produce
 $E_p =$

Due

$$E_s = -N \frac{d\phi}{dt}$$

$$\frac{E_p}{E_s} =$$

$$\frac{E_s}{E_p} =$$

$$\frac{E_s}{E_p} =$$

$$\frac{E_s}{E_p} =$$

$$\frac{N_s}{N_p} =$$

change in magnetic flux in primary will produce induced current

$$\mathcal{E}_p = -N_p \frac{d\phi}{dt} \rightarrow (1)$$

Due to change in secⁿ

$$\mathcal{E}_s = -N_s \frac{d\phi}{dt} \rightarrow (2)$$

Dividing (1) by (2)

$$\frac{\mathcal{E}_p}{\mathcal{E}_s} = \frac{N_p}{N_s}$$


$$\frac{\mathcal{E}_s}{\mathcal{E}_p} = \frac{N_s}{N_p} \quad \left[\frac{\mathcal{E}_s}{\mathcal{E}_p} = k \right]$$

$$\frac{N_s}{N_p} = k \rightarrow \text{Transformation ratio}$$

$$k > 1 \quad N_s > N_p \quad \mathcal{E}_s > \mathcal{E}_p$$

output volt > input volt

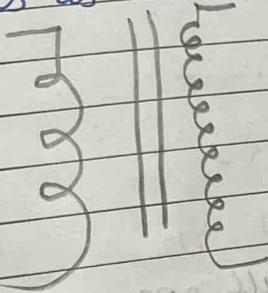
This is called step-up transformer (voltage ↑)



$$k < 1 \quad \frac{N_s}{N_p} < 1 \quad N_s < N_p \quad \mathcal{E}_s < \mathcal{E}_p$$

output volt < input volt

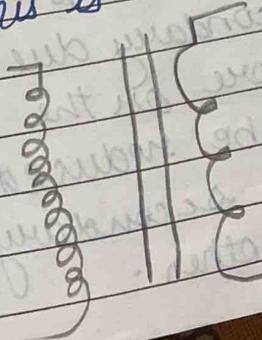This is called step-down transformer (voltage ↓)



Transformer is not a power device.

Input power = output power

$$E_p I_p = E_s I_s = \text{constant}$$

$$\frac{E_s}{E_p} = \frac{I_p}{I_s}$$

$$\boxed{E \propto \frac{1}{I}} \quad \text{Non-ohmic}$$

$$VI = K \\ V \propto \frac{1}{I}$$

Thus, a step up transformer changes low voltage high current to high voltage low current

A step down transformer converts high voltage low current to low voltage high current

Ideal transformer

Input power = output power

(efficiency) $\eta = \frac{E_s I_s}{E_p I_p}$

$$\boxed{\eta = 100\%}$$

Losses in transformer

$$\eta \neq 100\%$$

$$\eta = \frac{E_s I_s}{E_p I_p}$$

In actual transformers, small energy losses do occur due to the following reasons:-

- (i) Flux leakage: There is ^{always} some flux leakage; that is, not all of the flux due to primary passes through the secondary due to poor design of the core or the air gaps in the core. It can be reduced by winding the primary and secondary coils one over the other.

(ii) Resistance of the windings: The wire used for the windings has some resistance and so, energy is lost due to heat produced in the wire (I^2R). In high current, low voltage windings, these are minimised by using thick wire.

(iii) Eddy currents: The alternating magnetic flux induces eddy currents in the iron core and causes heating. The effect is reduced by using a laminated core.

(iv) Hysteresis: The magnetisation of the core is repeatedly reversed by the alternating magnetic field. The resulting expenditure of energy in the core appears as heat and is kept to a minimum by using a magnetic material which has a low hysteresis loss.

Ques. The primary coil of an ideal step-up transformer has 100 turns and the transformation ratio is also 100. The input voltage and power are 220V and 100W resp.

Calculate -

- (i) no. of turns in the secondary
- (ii) the current in the primary
- (iii) voltage across the secondary
- (iv) the current in the secondary
- (v) power in the secondary

Ques. A transformer of 100% efficiency has 200 turns in the primary and 40,000 turns in the secondary. It is connected to a 220V main supply and the secondary feeds to a $100\text{ k}\Omega$ resistance. Calculate

- the output potential diff. per turn
- total output pot. diff.
- power delivered to the load

Ans) $K = 100 = \frac{N_s}{N_p}$

$$N_p = 100$$

$$\frac{N_s}{N_p} = 100$$

$$(i) \quad N_s = 10,000$$

$$E_p = 220\text{V}$$

$$P_p = 1100\text{W}$$

$$P_p = E_p I_p$$

$$100 \cdot 1100 = 220 \times I_p$$

$$(ii) \quad I_p = \frac{1100}{220} = 5\text{A}$$

$$\frac{E_s}{E_p} = \frac{N_s}{N_p}$$

$$E_p = N_p$$

$$E_s = 100$$

$$220$$

$$(iii) \quad E_s = 22,000\text{V}$$

$$E_p I_p = E_s I_s$$

$$220 \times 5 = 22000 I_s$$

$$(iv) \quad I_s = \frac{1}{20}\text{A}$$

$$(v) \quad P_p = P_s$$

$$\text{Ans.} \quad \eta = 100\%$$

$$A \cdot C$$

USE: It is and out

PRINCIPLE: an in neric Ind

CONSTRUCTION

N

slip rings

(v)

$$P_p = P_s$$

$$P_s = 1100 \text{ W}$$

Ans.


$$\eta = 100\%$$

A.C. Generator

USE: It is used to produce alternating current and alternating voltage

PRINCIPLE: Whenever magnetic flux is changed, an induce current is produced (Electromagnetic Induction)

CONSTRUCTION:

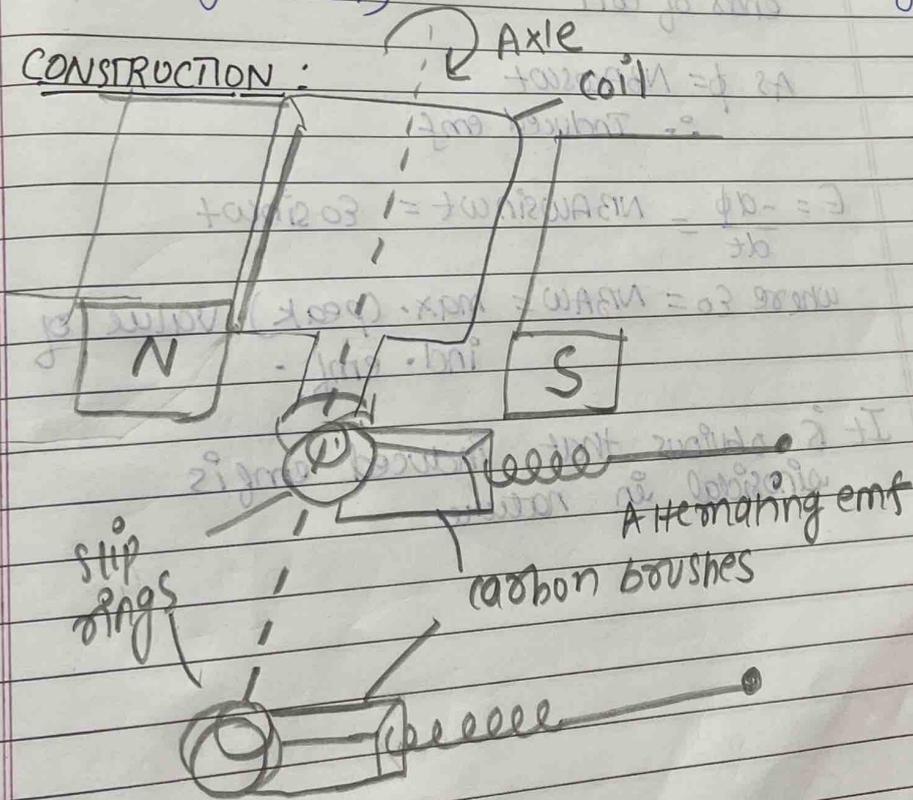

Working
 When an armature coil of N turns and each turn enclosing area A is placed in a uniform mag. field of strength B making an angle θ from normal to the direction of magnetic field, mag. flux linked with the coil is $\phi = NBA \cos \theta$. As the coil is rotated about its own axis with an ang. speed ω then value of angle $\theta = \omega t$ and hence, mag. flux changes and an induced emf is developed across the ends of coil

As $\phi = NBA \cos \omega t$
 \therefore Induced emf

$$E = -\frac{d\phi}{dt} = NBA\omega \sin \omega t = \epsilon_0 \sin \omega t$$

where $\epsilon_0 = NBA\omega = \text{max. (peak) value of ind. emf.}$

It is obvious that induced emf is sinusoidal in nature

NumericalsQ1.

In a LCR circuit $L=100\text{mH}$, $C=10\mu\text{F}$, $R=40\Omega$ is connected to 220V , 50Hz A.C.

- Find (i) ν at resonance
 (ii) Z at "
 (iii) I at "

$$(i) \omega_0 L = \frac{1}{\omega_0 C}$$

$$\nu_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\nu_0 = \frac{1}{2\pi\sqrt{100 \times 10^{-3} \times 10 \times 10^{-6}}}$$

$$\nu_0 = \frac{1000}{2\pi} = \frac{500}{\pi} \text{ Hz}$$

$$(ii) Z = R = 40\Omega$$

$$(iii) E\nu = I\nu Z$$

$$220 = I\nu 40$$

$$I\nu = \frac{220}{40} = \frac{11}{2} = 5.5\text{A}$$

Q2.

$L=100\text{mH}$, $R=10\Omega$ and C connected to 200V AC, $\nu=50\text{Hz}$. Find C if phase angle b/w V and I is zero.

Ans.LCR

($\phi=0^\circ$)
 Resonance

$$\nu=50\text{Hz}$$

$$L=100 \times 10^{-3}\text{H}$$

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$C = \frac{1}{\omega^2 L}$$

$$C = \frac{1}{(2\pi\nu)^2 L}$$

$$C = 1$$

$$2\pi \times 50 \times 50 \times 2\pi \times 10^{-5}$$

$$C = \frac{1}{10 \times 2 \times 2 \times 2500 \times 10^5}$$

$$C = \frac{1}{40 \times 2500 \times 10^5} = \frac{1}{10^{10}} \text{ F}$$

Q3.

CR circuit connected to A.C. Voltage across C and R are 120V, 90V resp. If rms

current in circuit is 3A. find Z, power factor.

Ans.

$E_C = 120\text{V}$ $E_R = 90\text{V}$ $I_V = 3\text{A}$ (series \rightarrow same current)

$$E_C = I_V \times X_C$$

$$120 = 3 \times X_C \quad \boxed{X_C = 40 \Omega}$$

$$E_R = I_V \times R \quad 90 = 3R$$

$$\boxed{R = 30 \Omega}$$

$$Z = \sqrt{X_C^2 + R^2}$$

$$Z = \sqrt{1600 + 900} \quad \boxed{Z = 50 \Omega}$$

$$\cos \phi = \frac{R}{Z}$$

$$= \frac{30}{50}$$

$$\boxed{\cos \phi = \frac{3}{5}}$$

Phase angle $\rightarrow \phi$

Q4. =

Power factor of a circuit is $1/2$. Find phase angle b/w V and I ?

$$\cos \phi = \frac{1}{2} \quad \boxed{\phi = 60^\circ} = \pi/3$$

Ans. =

Q5. =

An inductor and a resistor are connected across $12V, 50Hz$ and a current of $0.5A$ flows. If phase diff b/w V and I is $\pi/3$. Find impedance and resistance.

Ans. = $LR \quad I = 0.5A \quad Z = ? \quad V = 50Hz$
 $V = 12V \quad \phi = \pi/3 \quad \delta = ?$

$$Z = \sqrt{X_L^2 + R^2}$$

$$V = IZ$$

$$12 = \frac{1}{2} Z$$

$$\boxed{Z = 24\Omega}$$

$$Z = \sqrt{X_L^2 + R^2}$$

$$24 = \sqrt{4R^2}$$

$$\boxed{R = 12\Omega}$$

or

$$\cos \phi = \frac{R}{Z}$$


$$\frac{\pi}{3} = \frac{R}{24}$$

$$\frac{24\pi}{3} = R$$

$$\tan \phi = \frac{X_L}{R}$$


$$\sqrt{3} = \frac{X_L}{R}$$

$$X_L = \sqrt{3}R$$

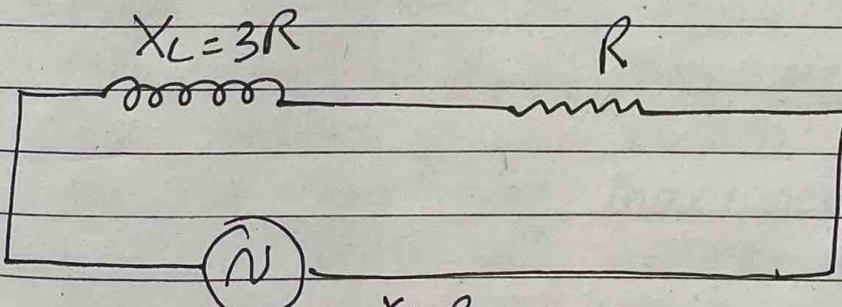

(a)

Ratio of power factor in a to b.

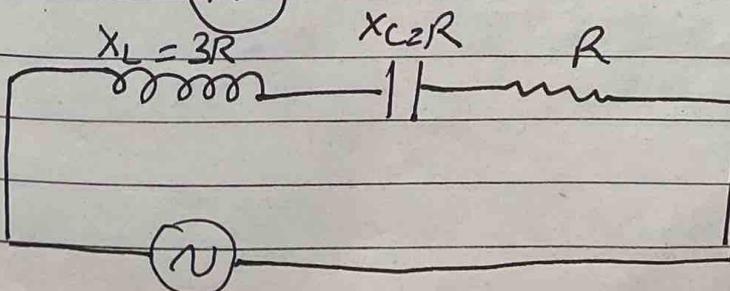

(b)

Q6. =

Solⁿ.

$$Z_1 = \sqrt{(X_L)^2 + R^2}$$

$$Z_1 = \sqrt{(3R)^2 + R^2}$$

$$Z_1 = \sqrt{9R^2 + R^2}$$

$$Z_1 = \sqrt{10R^2}$$

$$Z_1 = \sqrt{10} R$$

$$Z_2 = \sqrt{(X_L - X_C)^2 + R^2}$$

$$Z_2 = \sqrt{(3R - R)^2 + R^2}$$

$$Z_2 = \sqrt{4R^2 + R^2}$$

$$Z_2 = \sqrt{5R^2}$$

$$Z_2 = \sqrt{5} R$$

$$\cos \phi_1 = \frac{R}{Z_1}$$

$$\cos \phi_2 = \frac{R}{Z_2}$$


$$\cos \phi_1 = \frac{R}{\sqrt{10}R}$$

$$\cos \phi_2 = \frac{R}{\sqrt{5}R}$$

$$\cos \phi_1 = \frac{1}{\sqrt{10}}$$

$$\cos \phi_2 = \frac{1}{\sqrt{5}}$$
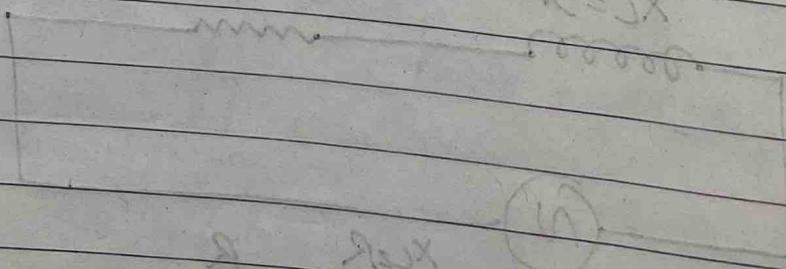
$$\frac{\cos \phi_1}{\cos \phi_2} = \frac{1}{\sqrt{2}}$$



Q.

A capacitor of unknown capacitance, a resistor of 100Ω , and an inductor of self-inductance $L = 4 \text{ H}$ are connected in series to an a.c. source of 200 V and 50 Hz . Calculate the value of capacitance and the current that flows in the circuit when the current is in same phase w/ the voltage.

Resonance

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$C = \frac{1}{\omega^2 L}$$

$$C = 25 \mu\text{F}$$

$$Z = R$$

$$Z = 100 \Omega$$

$$V = 200 \text{ V}$$

$$V = I Z$$

$$200 = I \times 100$$

$$I = 2 \text{ A}$$

In this find I_r only.

$$I_r = \frac{I_0}{\sqrt{2}}$$

$$I_0 = 2\sqrt{2}$$

Q.

Imp.

When an inductor is connected to a 200 V d.c. voltage, a current of 1 A flows through it when the same inductor is connected to a 200 V , 50 Hz ac source only. 0.5 A current flows. Explain why? Also calculate the self inductance of inductor. Whenever inductor is connected w/ d.c. voltage, it behave as resistor

$$R = \frac{V}{I} = \frac{200}{1} = 200 \Omega$$

Same inductor w/ ac :- LR circuit

$$R = 200 \Omega$$

$$I = 1 \text{ A}$$

$$R = 400 \Omega$$

$$I = \frac{1}{2} \text{ A}$$

PAGE NO.:

$$\epsilon v = I v Z$$

$$\therefore Z = \frac{\epsilon v}{I v} = \frac{200}{\frac{1}{2}} = \boxed{400 \Omega}$$

As resistance \uparrow , $I \downarrow$

$$Z = \sqrt{X_L^2 + R^2}$$

$$(400)^2 = X_L^2 + (200)^2$$

$$X_L^2 = 120000$$

$$X_L = \sqrt{120000}$$

$$X_L = \omega L$$

$$X_L = 2\pi \nu L$$